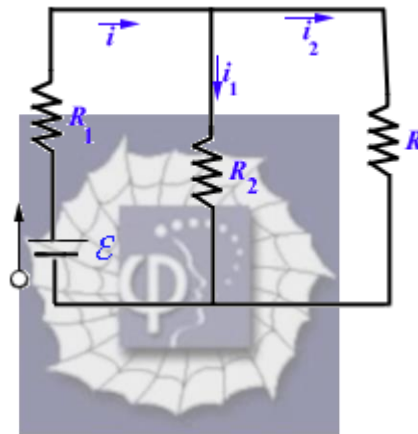


408.

Problem 33.26 (RHK)

In the circuit shown in the figure E , R_1 , and R_2 have constant values but R can be varied. We have to find an expression for R that results in the maximum heating in that resistor.



Solution:

We will find the current flowing through R . We have a multi-loop circuit with one junction. Equations that follow from Kirchhoff's laws are

$$i = i_1 + i_2,$$

$$i = \frac{E}{R_1 + \frac{RR_2}{R + R_2}} = \frac{E(R + R_2)}{R_1R_2 + R(R_1 + R_2)}.$$

Also,

$$\begin{aligned} i_2 R &= i_1 R_2 \\ &= (i - i_2) R_2, \end{aligned}$$

or

$$i_2 = \frac{i R_2}{R + R_2} = \frac{E R_2}{R_1 R_2 + R(R_1 + R_2)}.$$

Rate of Joule heating in the resistance R is

$$P = i_2^2 R = \left(\frac{E R_2}{R_1 R_2 + R(R_1 + R_2)} \right)^2 R.$$

We find the extremum solution of $P(R)$ by requiring

$$\left. \frac{dP(R)}{dR} \right|_{R=R_{\max}} = 0.$$



This condition gives the equation

$$\frac{E^2 R_2^2}{(R_1 R_2 + R_{\max}(R_1 + R_2))^2} - \frac{2E^2 R_2^2 R_{\max}(R_1 + R_2)}{(R_1 R_2 + R_{\max}(R_1 + R_2))^3} = 0.$$

As

$$R_1 R_2 + R_{\max}(R_1 + R_2) \neq 0,$$

we have

$$R_1 R_2 + R_{\max}(R_1 + R_2) - 2R_{\max}(R_1 + R_2) = 0,$$

or

$$R_{\max} = \frac{R_1 R_2}{R_1 + R_2}.$$